


Memory-mapped External Peripherals II

ECE 3710

I have had a perfectly
wonderful evening, but
this wasn't it.

- Groucho Marx

external memory mapping:

 

1. data written to uC memory
is sent to external device
2. data read from uC memory
comes from external device

uC is configured to handle:


1. timing
2. pin assignments for data/addr
3. sending data/addr
4. receiving data

result: external device
appears local

(reads write don't require your code to set/read pins directly)

ARM memory map

which addresses
point to which things

 


writes here directed
at external devices

addr sent on i/o pins;
data sent/recv on i/o pins

EPI: 8-bit demultiplexed mode

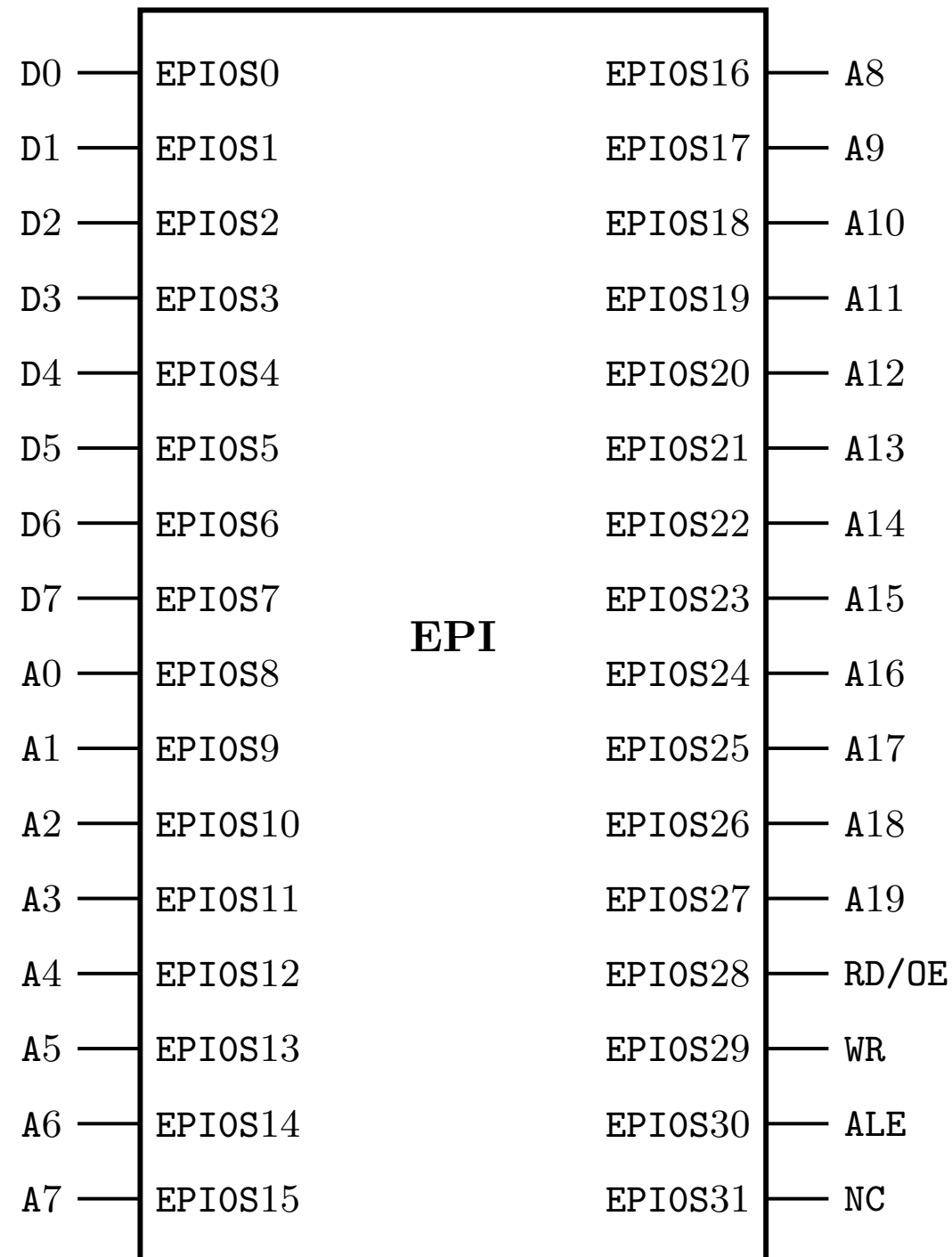
8-bits
address and data
↓
 2^{20} of something
(doesn't have to be bytes)



$D[7:0] = \text{DATA}[7:0]$ ← first byte of data

$A[19:0] = 0xA00[00000]$ ← written here

example: SRAM

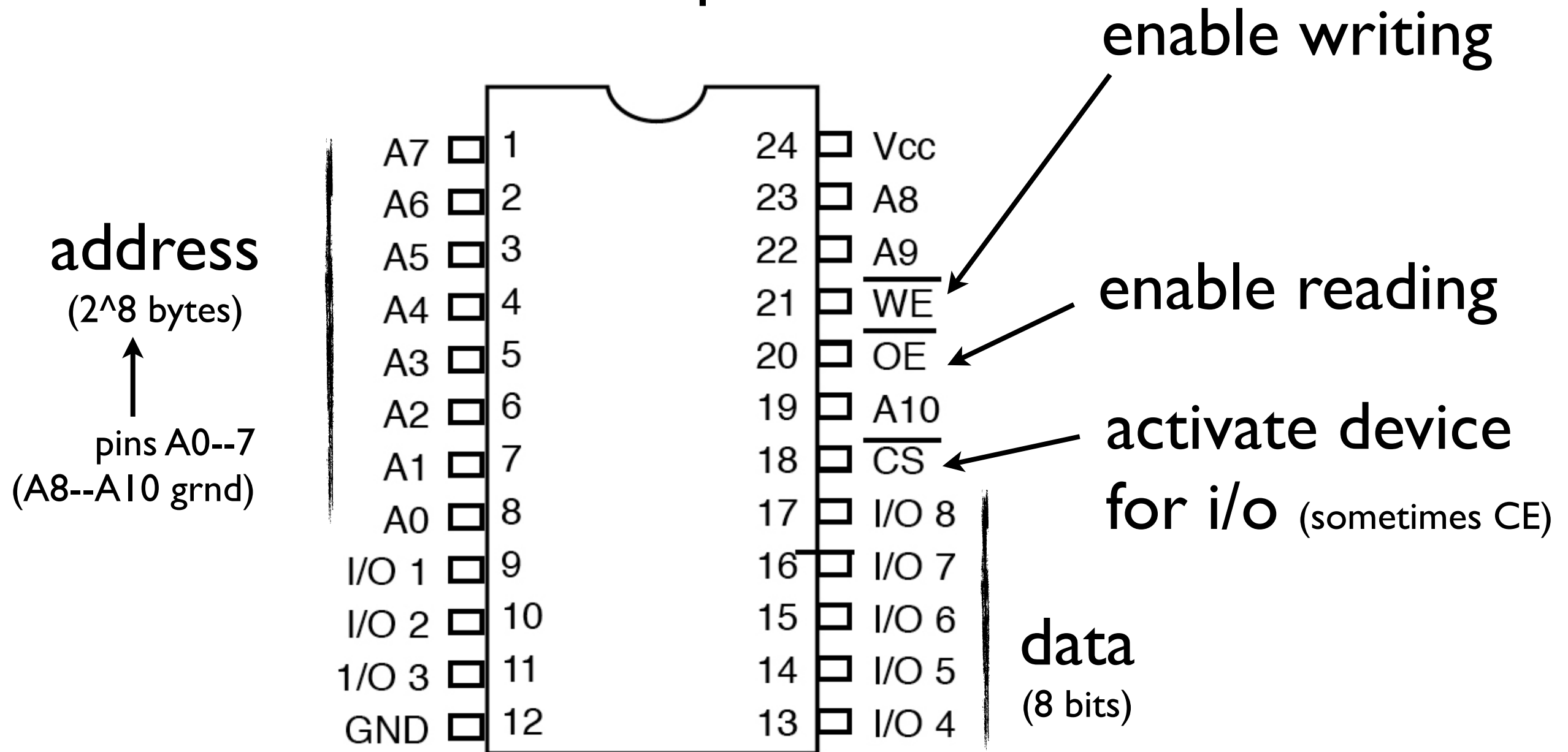

write 0xAA to address 0x34:

SRAM needs
to see
(at same time)

$A[7:0] = 0x34$
 $I/O[7:0] = 0xAA$
 $CS=0, WE=0$

example: SRAM

(old way)


write 0xAA to address 0x34:

$PA[7:0] = 0x34$

$PB[7:0] = 0xAA$

$PC1 = 0, PC2 = 0$

our routine

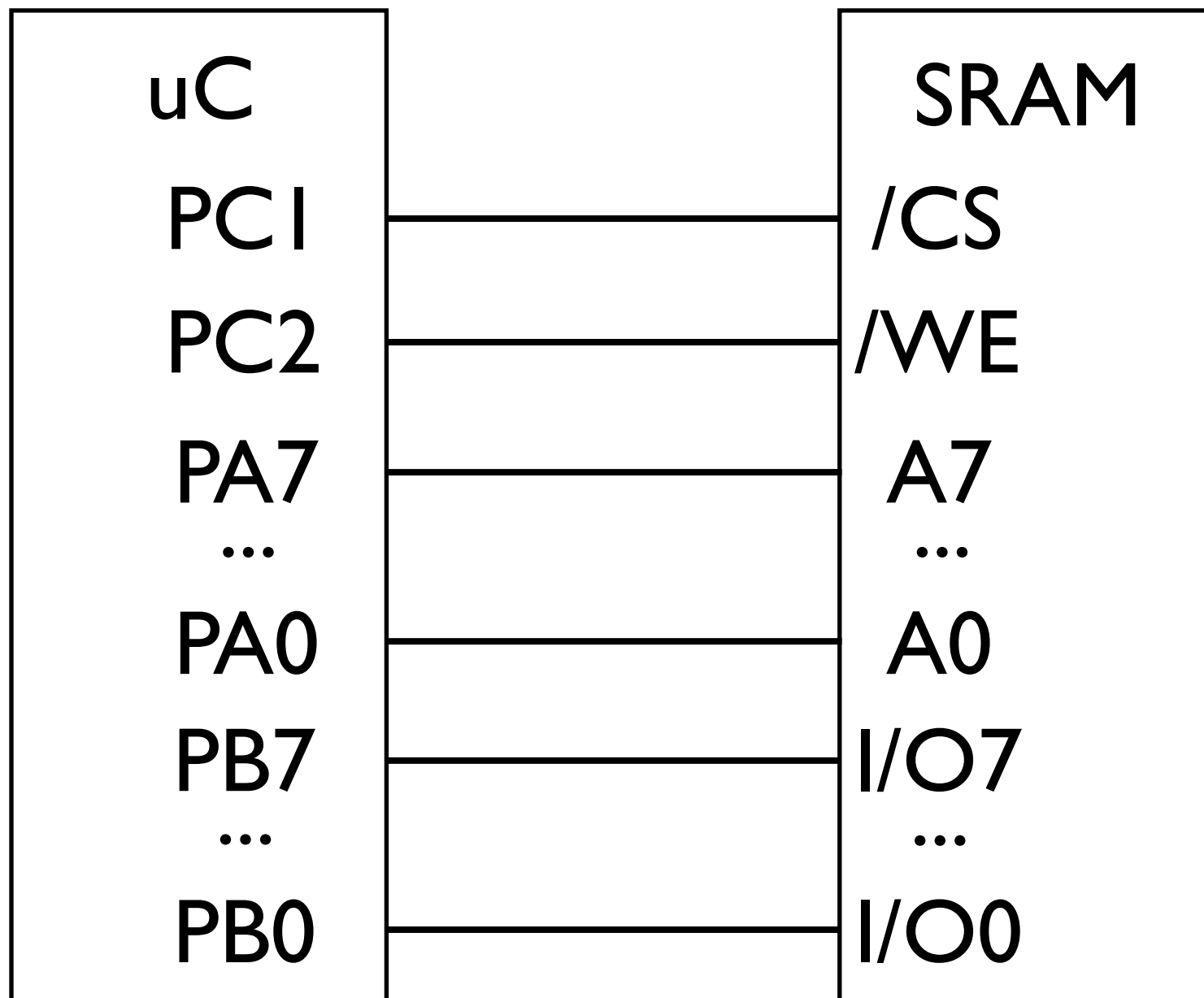

ex: uC configured for mm with 256x8 device

addr: 8 bits
data: 8 bits

write 0xAA to
0xA0000034

a write to mm location:

$l.addr = 0xA0000034 \ \& \ 0xFF = 0x34$

$l.data = 0xAA \ \& \ 0xFF = 0xAA$

what device will see
(bits uC sets on pins)


example: SRAM

(mm way)

our routine



write 0xAA to address
0xA0000034

 


uC does



EPIOS[15:8]=0x34
EPIOS[7:0]=0xAA
EPIOS16=0,
EPIOS29=0

EPI: 8-bit multiplexed mode

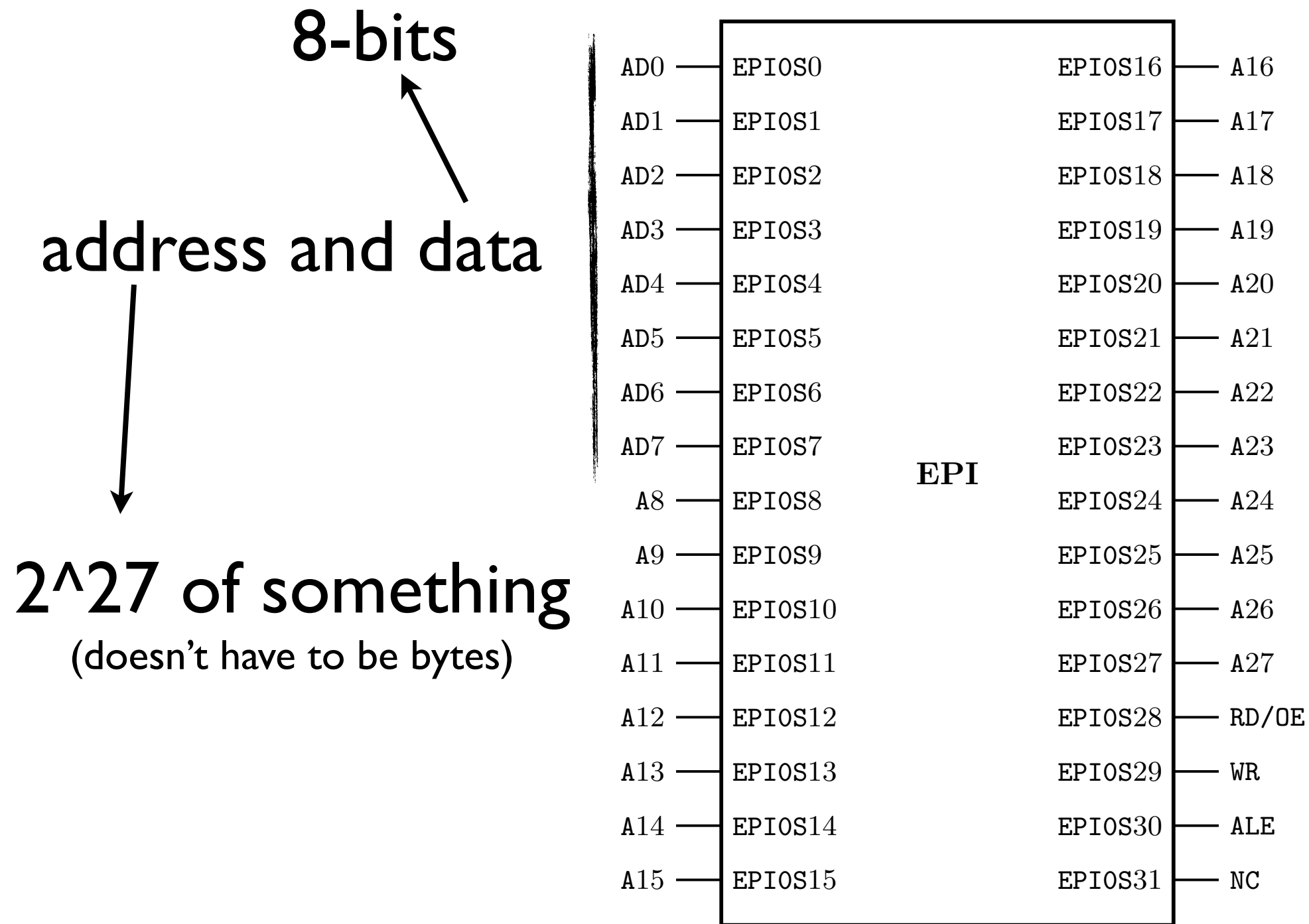

$AD[7:0] = 0xA00000[00]/DATA[7:0]$


$A[27:8] = 0xA[00000]00$

memory map

(multiplexed)

if base external mm addr: 0xA0000000

Q: which addr correspond
to device?

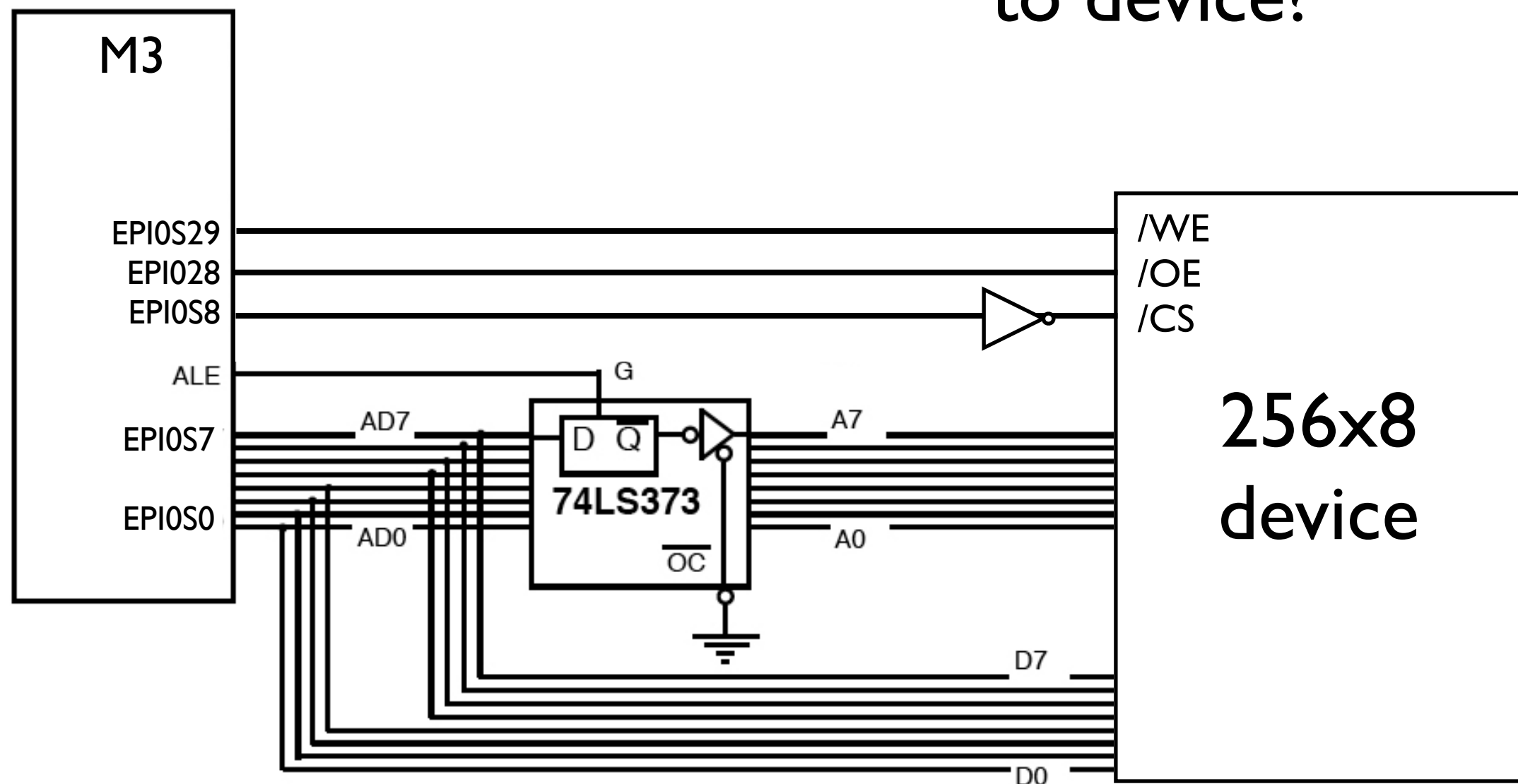


memory map

Q: which addr correspond
to device?

to address device: 9 bits

a. eight for data addr

b. one for CS

 

memory map

Q: which addr correspond
to device?

offsets for device:

0b100000000 -- 0b111111111

0x100 -- 0x1FF

for CS pin



device has addresses: 0xA0000100 -- 0xA00001FF

reading/writing to (MM) device in C

to make this work:

var. needs to be located/point to location
in external memory



when data is assigned to var, uC puts it at the
location or the location pointed at

ex: MM devices and C

(write 0xAA to address 0x34)

```
unsigned char X __attribute__((at(0xA0000134)));
```

```
void main()
```

```
{  
    X = 0xAA;           →   ldr    R1,=0xA0000134  
                           mov    R0,#0xAA  
                           str    R0,[R1]
```

ports/pins
activated as
before

stores 0xAA in external memory at 0x34

ex: simple way to access memory of device

use pointer \longrightarrow then device appears as array

```
unsigned char *DEV = (unsigned char *) 0xA0000100;
```

```
void main()
```

```
{
```

```
    unsigned char i;
```

```
    /* write 0...255 in external memory at 0x0 to 0xFF */
```

```
    for(i = 0; i < 255; i++)
```



```
        DEV[i] = i;
```

```
}
```


Q: what if multiple devices?

(shared bus)

#bits for
address = 14
 $16K = 2^{14}$

  


require 14 addr lines; have 28

a response:




but not the right one

Q: what if multiple devices?

 

AI:

← connect CS to extra addr pins

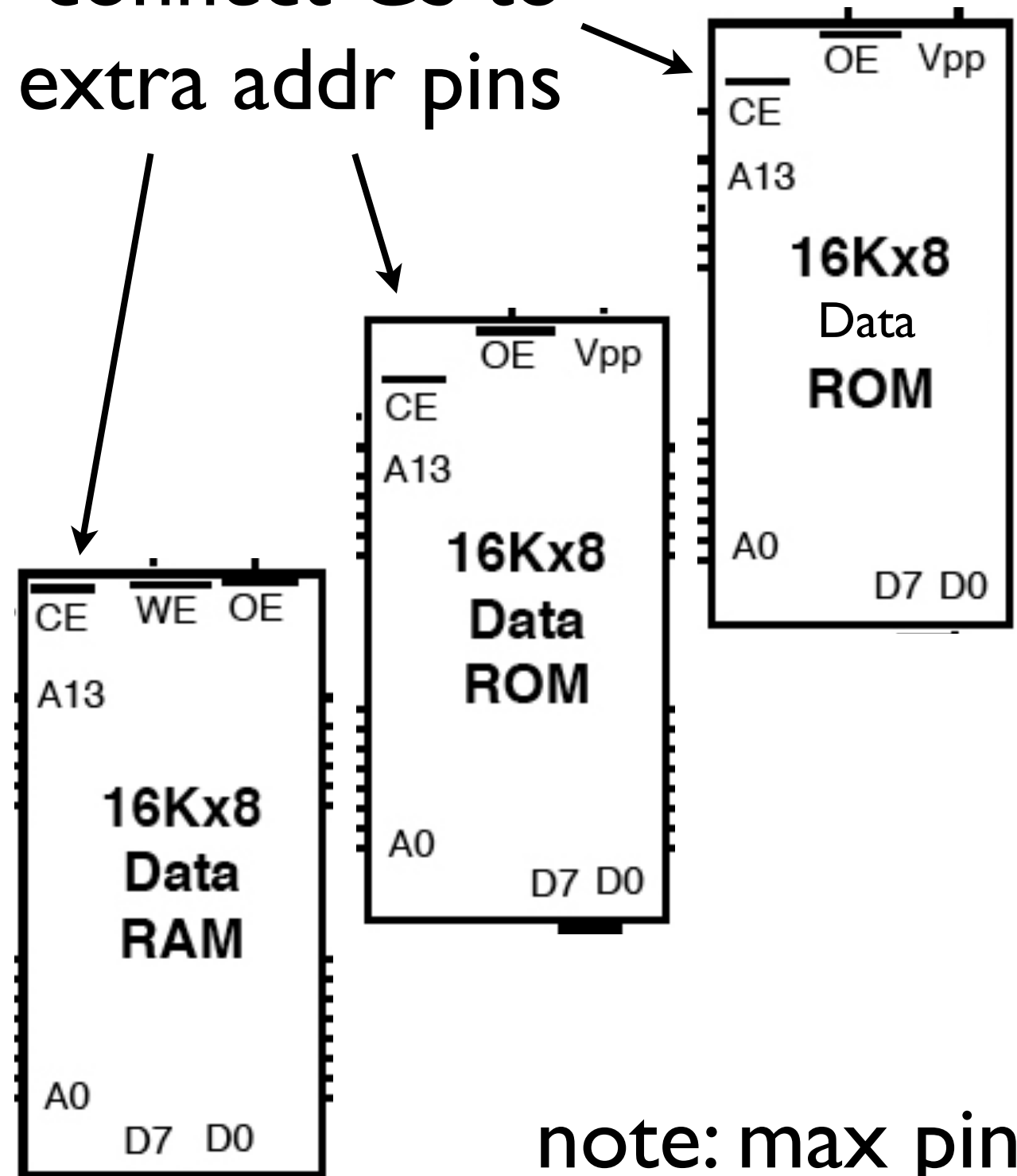


note: max pins

Q: what if multiple devices?

A2: decoder (minimise pins)

Block Diagram

 


Function Table

Inputs				Outputs								
Enable		Select										
G1	G2	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	L	H	H	H	H	H	H	L	H	H
H	L	H	H	L	H	H	H	H	H	H	L	H
H	L	H	H	H	H	H	H	H	H	H	H	L


multiple devices

(2-bit decoder)

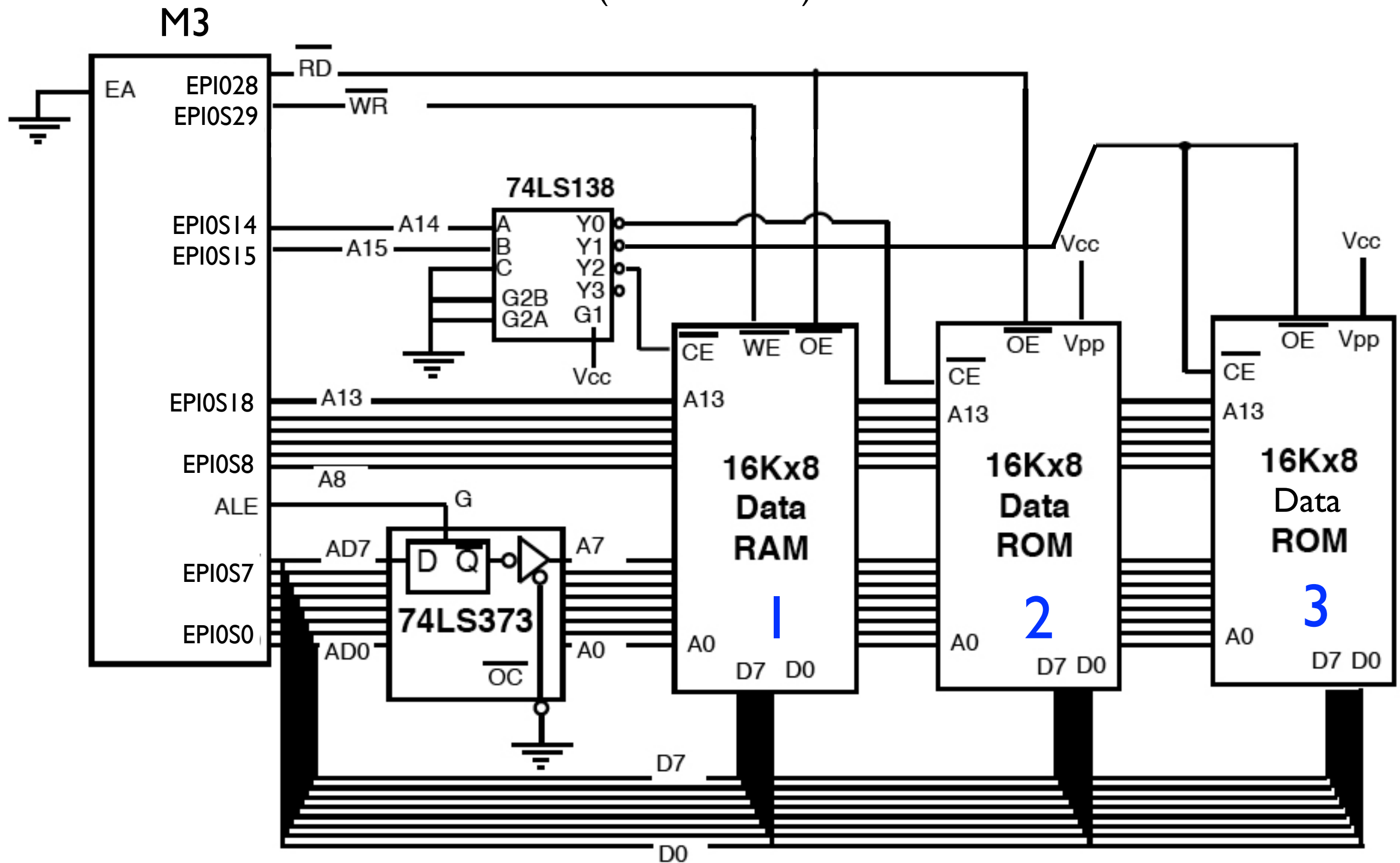

which addresses correspond to which device?

which bit combinations
activate devices?

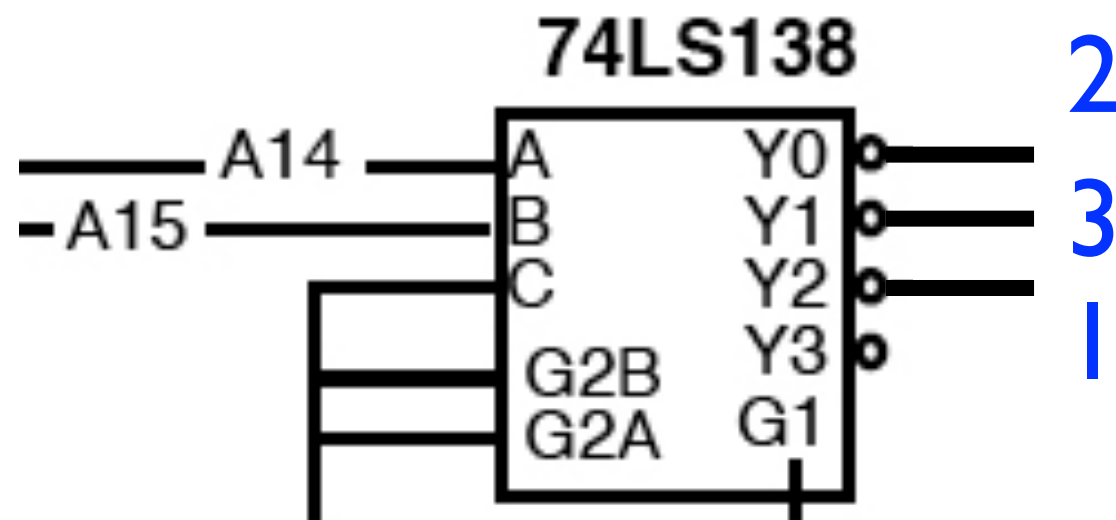

when $A[15:14] = [10]$ \longrightarrow device 1 on

when $A[15:14] = [00]$ \longrightarrow device 2 on

when $A[15:14] = [01]$ \longrightarrow device 3 on

when $A[15:14] = [10] \longrightarrow$ device 1 on


offsets

(from 0xA0000000)

when $EPIOS[15:0]: 0b1000000000000000$ to
 $0b1011111111111111$

write to

(0xA0008000---0xA000BFFF)

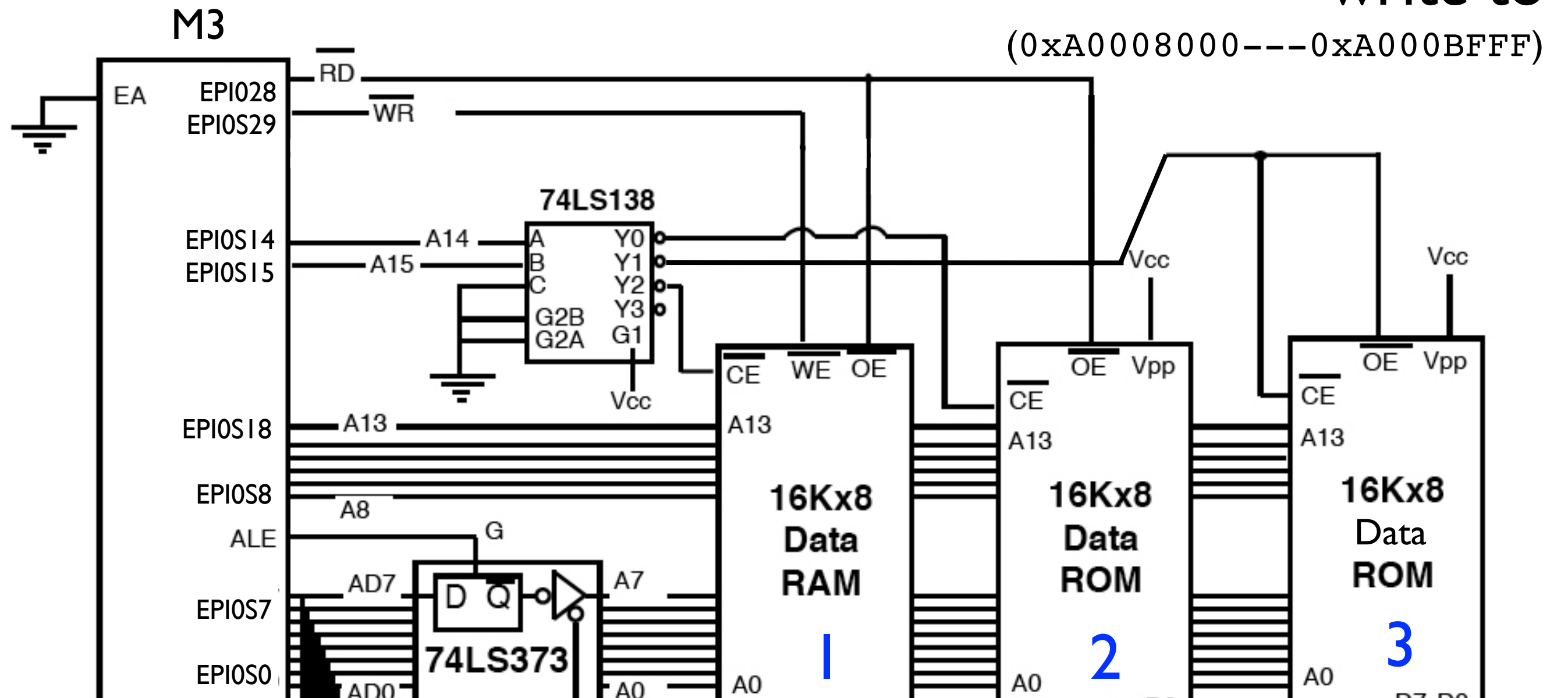

when $A[15:14] = [00] \longrightarrow$ device 2 on


offsets

(from 0xA0000000)

when $EPIOS[15:0]: 0b0000000000000000$ to
 $0b0011111111111111$

write to

(0xA0000000---0xA0003FFF)

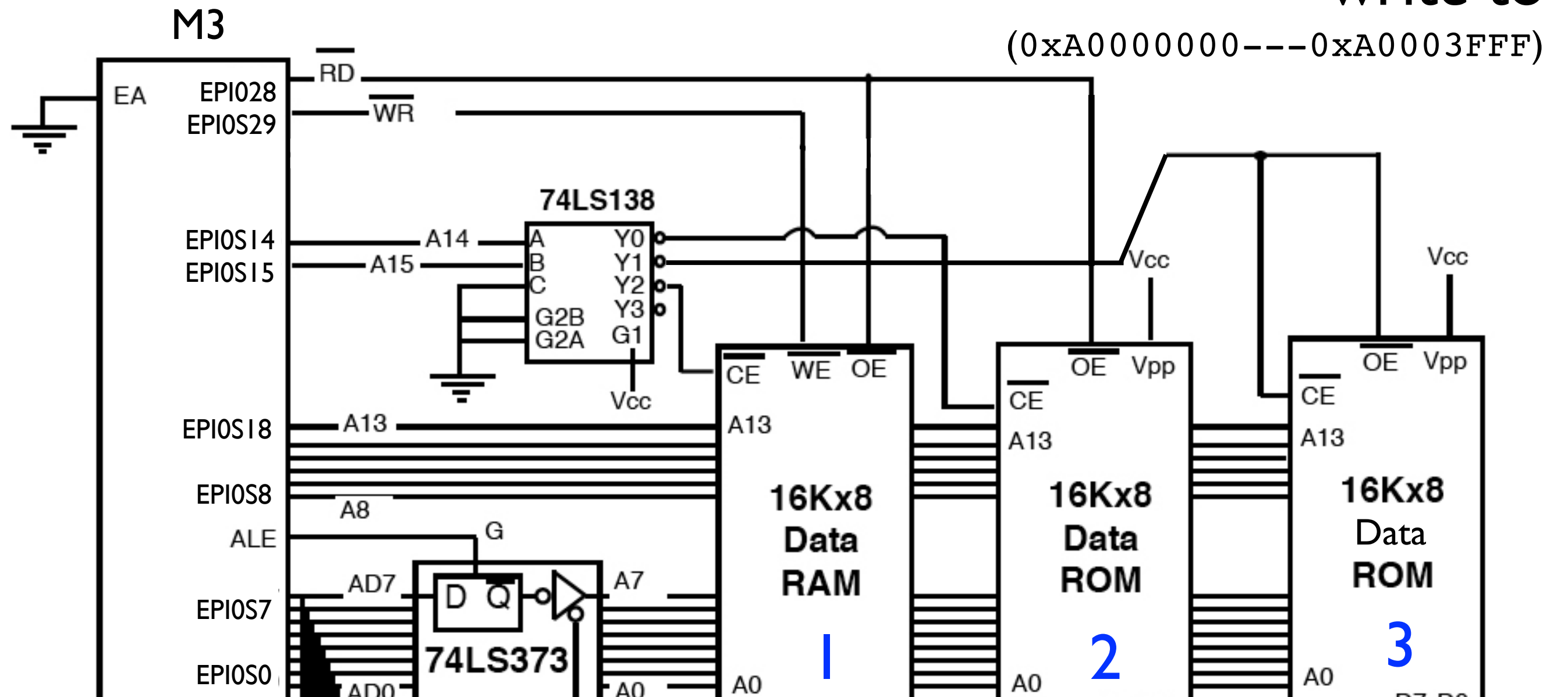

when $A[15:14] = [01] \longrightarrow$ device 3 on


offsets

(from 0xA0000000)

when $EPIOS[15:0]: 0b0100000000000000$ to
 $0b0111111111111111$

write to

(0xA0004000---0xA0007FFF)

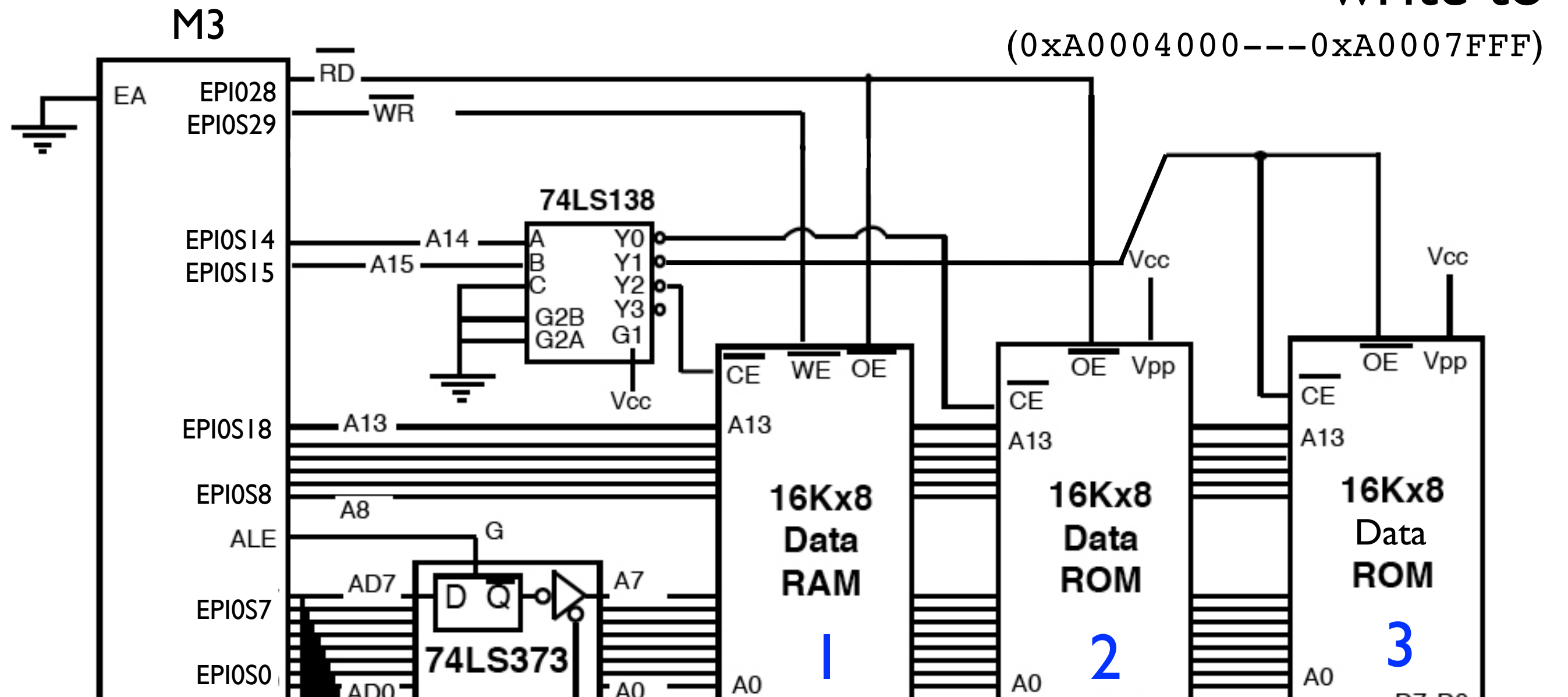


ex: simple way to access memory of multiple devices

min addr for device 1:

0b100000000000000000000000=0x8000

pointers to devices

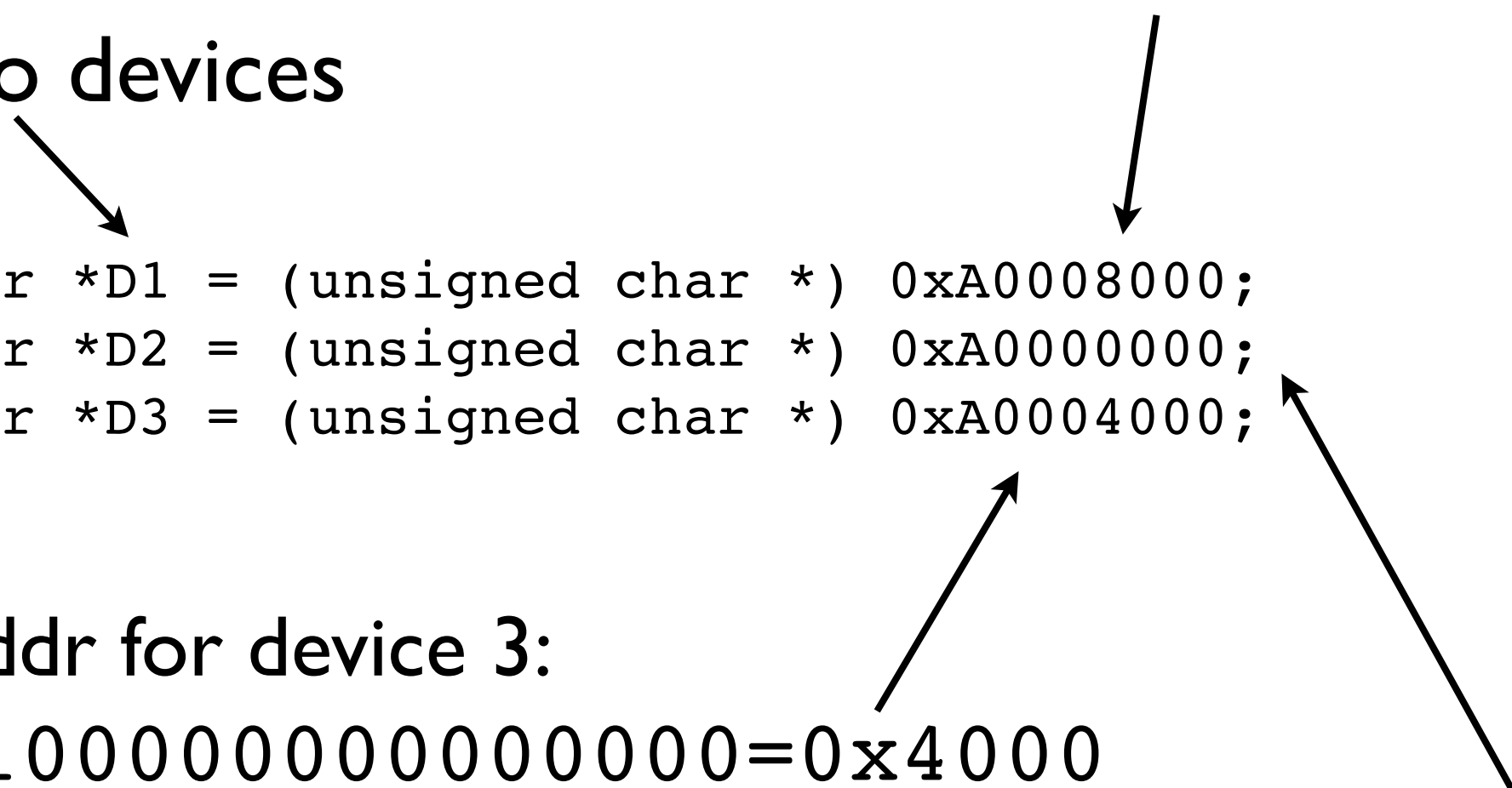

```
unsigned char *D1 = (unsigned char *) 0xA0008000;  
unsigned char *D2 = (unsigned char *) 0xA0000000;  
unsigned char *D3 = (unsigned char *) 0xA0004000;
```

min addr for device 3:

0b010000000000000000000000=0x4000


access device:

`Dx[0x0--0x3FFF]`

min addr for device 2:

0b000000000000000000000000=0x0000

Q: how can we memory map a DAC?

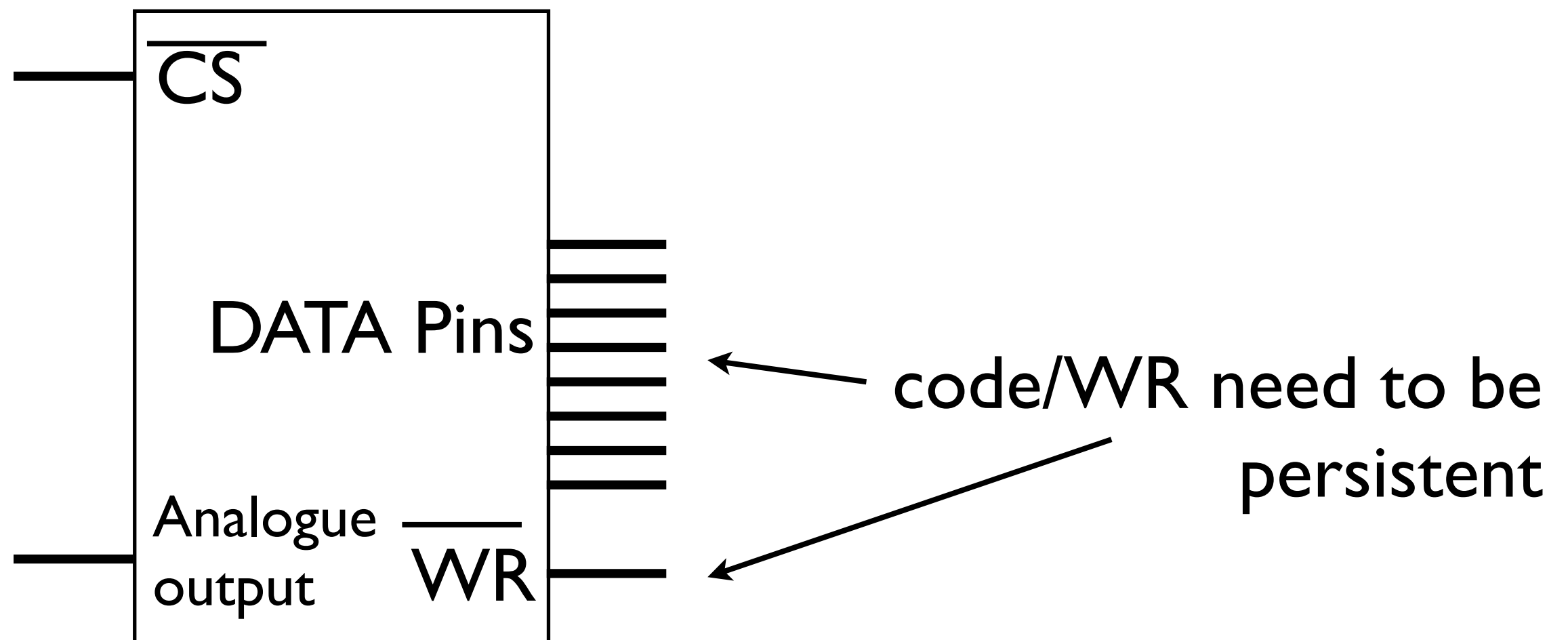

Q: how can we memory map a DAC?



A:

  1. get DAC with memory
2. have something retain code/WR for us

remember: uC only keeps data on
pins temporarily




ex: mm a dac
(on shared, multiplexed bus)



Funtion Table

Output control	Enable		Output
	G	D	
L	H	H	H
L	H	L	L
L	L	X	Q0
H	X	X	Z

 


ex: mm a dac

(on shared, multiplexed bus)

dac:


1. WR to ground
2. CS to ground

(always enabled, always outputting)

 

latch:

 1. G(enable) to A8
2. xD (latch) to databus
3. xQ (latch) to dac input




Function Table

Output control	Enable		Output
	G	D	
L	H	H	H
L	H	L	L
L	L	X	Q0
H	X	X	Z

ex: mm a dac


(on shared, multiplexed bus)

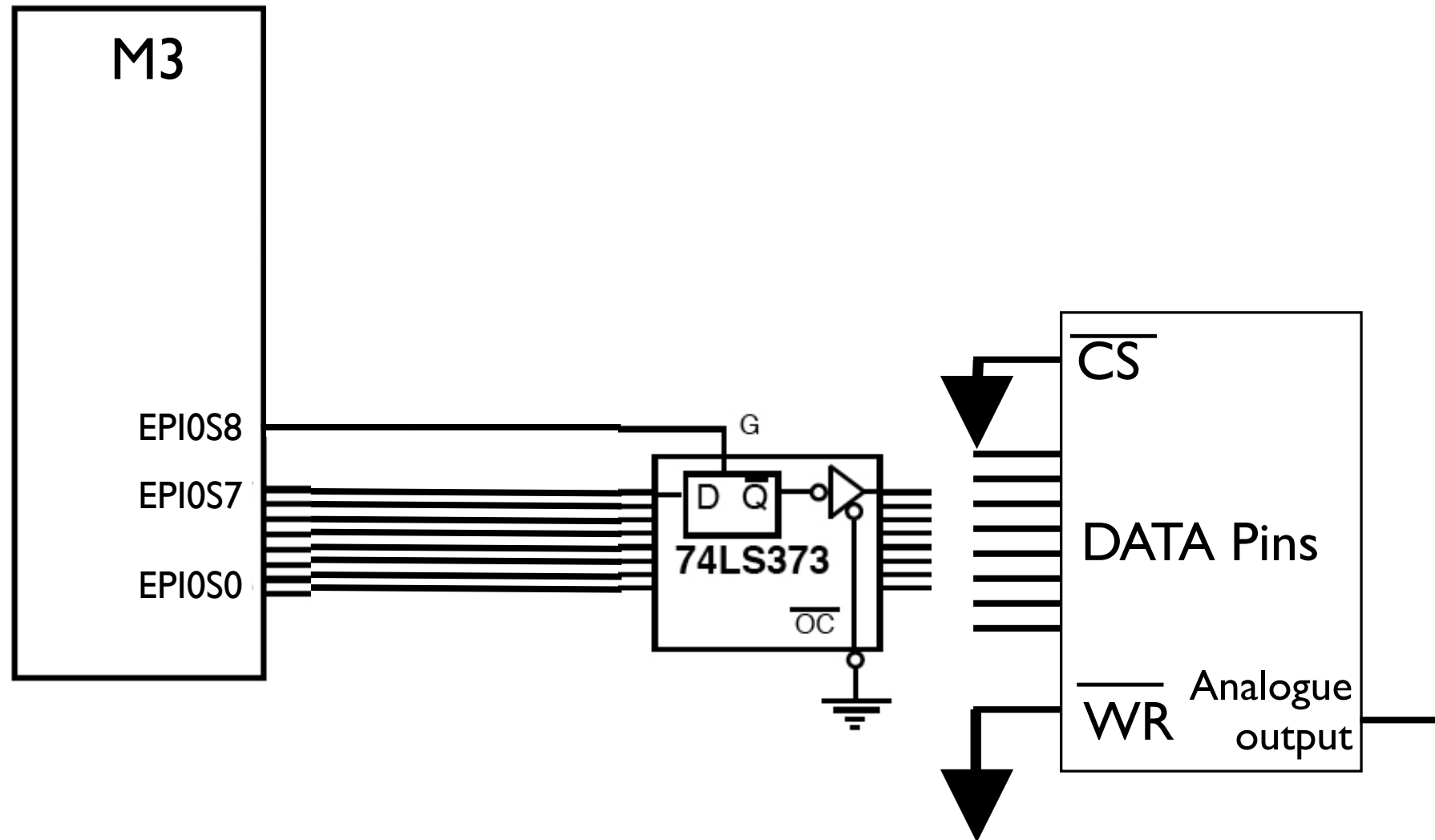

mm EPIOS[8:0]: 0b100000000 to
0b11111111


```
unsigned char DAC __attribute__((at(0xA0000100)));
```

```
DAC = 'Z';
```

 


0x5A=90

can we do it without multiplexing?

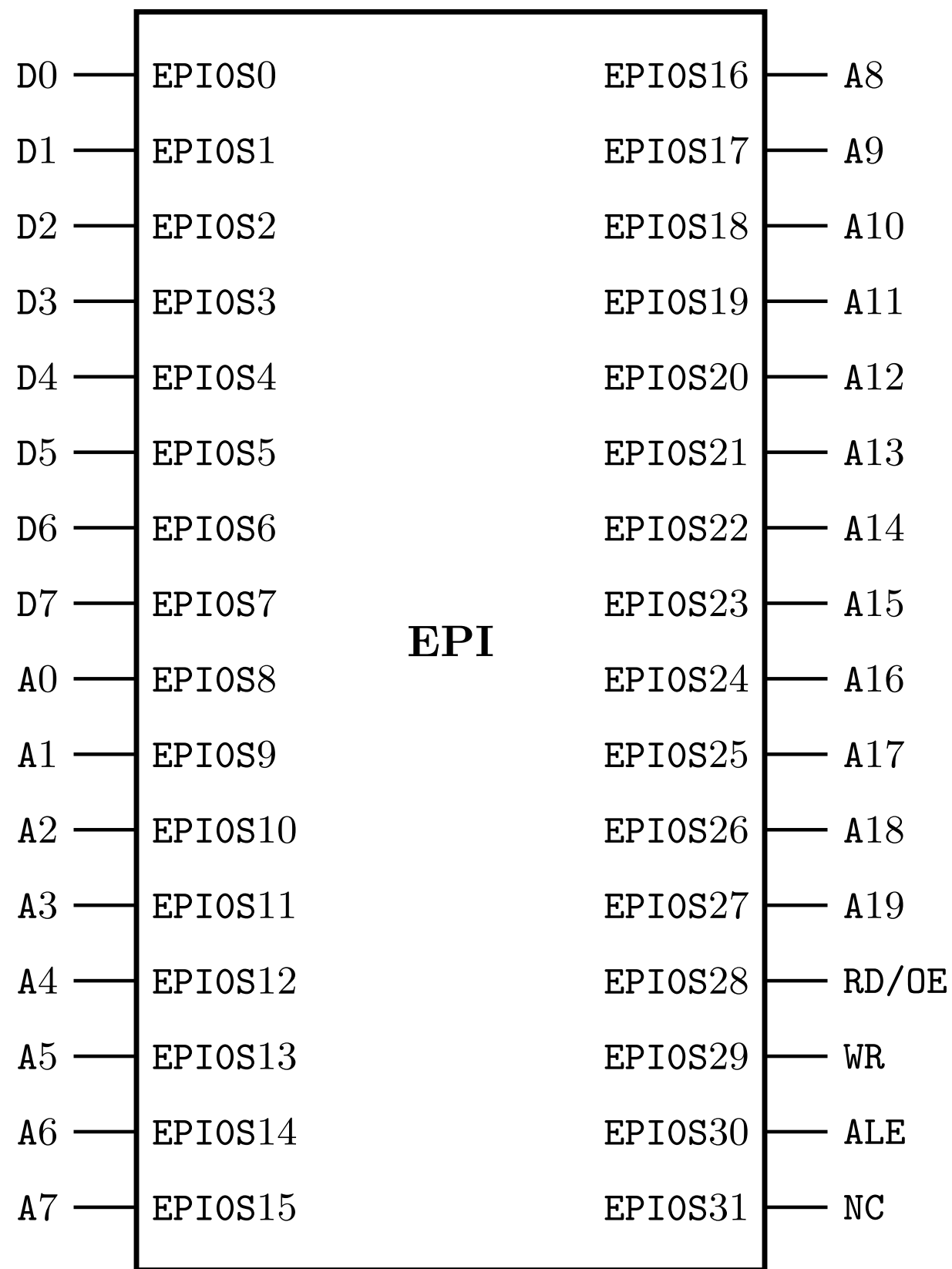


addr:0x10

 


Funtion Table

Output control	Enable		Output
	G	D	
L	H	H	H
L	H	L	L
L	L	X	Q0
H	X	X	Z

 


DAC without multiplexing

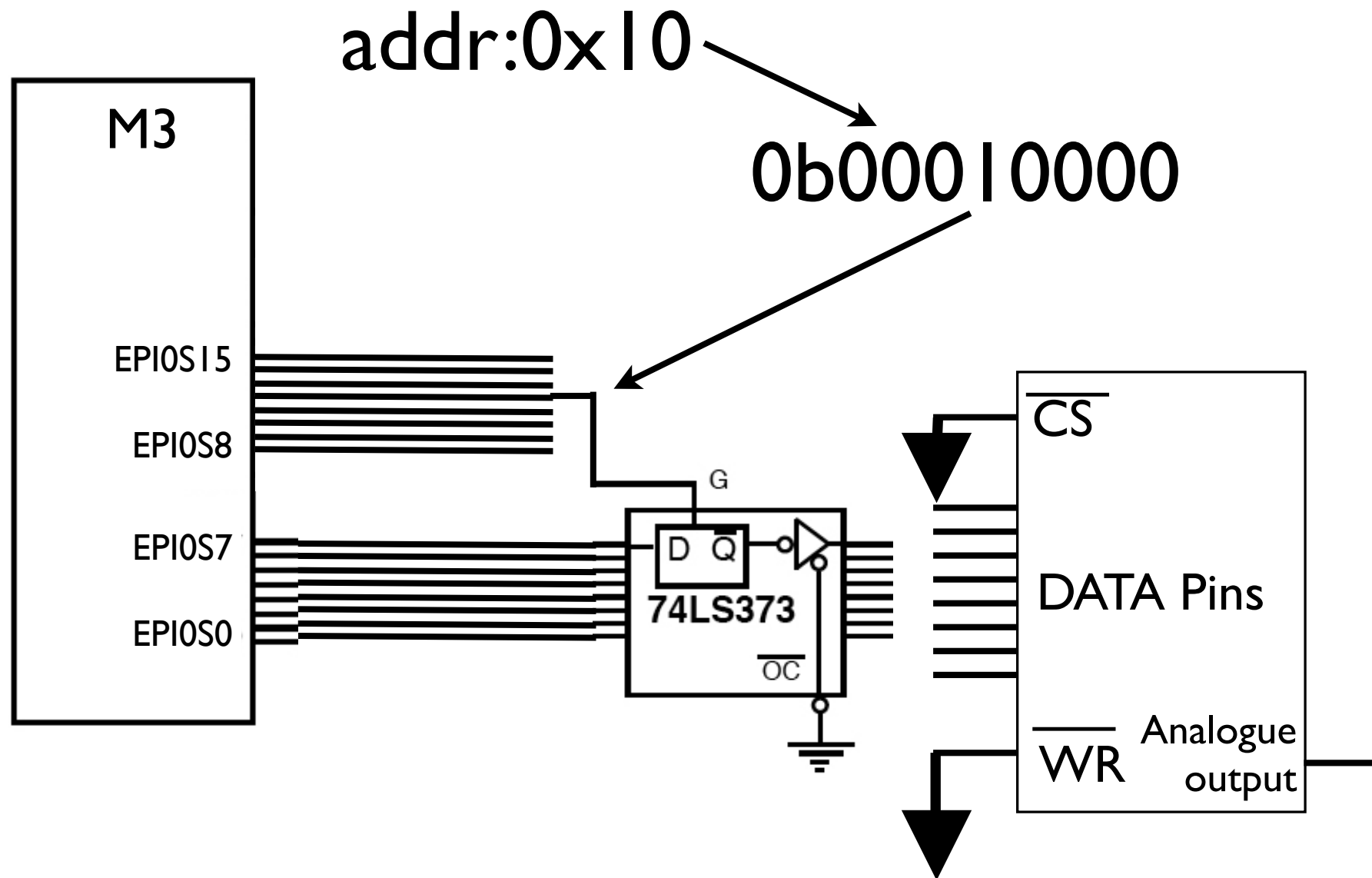

```
unsigned char DAC __attribute__((at(0xA0000010)));
```

```
DAC = 'Z';
```

mm of LCD (demultiplexed)

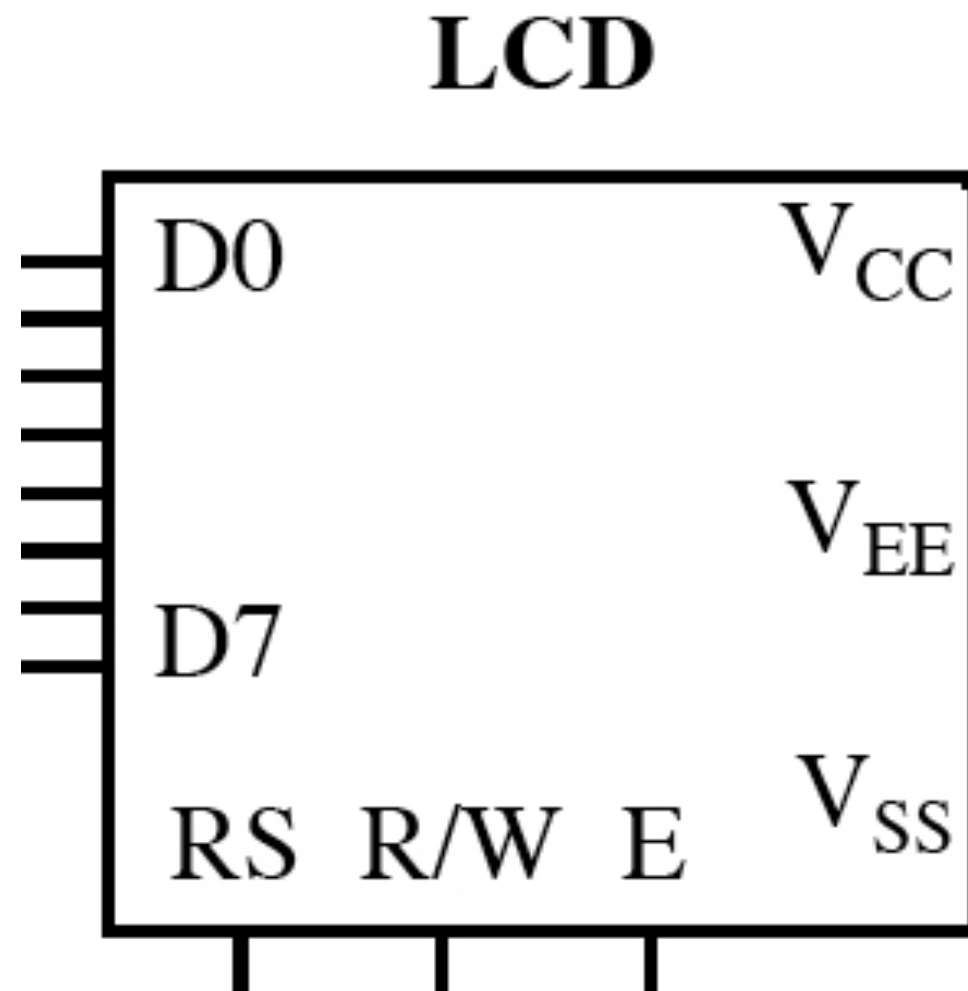

command or chars

D0 : D7 => 'data'

RS => D0:D7 is

0 command

1 data

RW => from LCD

0 write

1 read

E => CS/CE

these must be set for each communication